



# Sethu Senthil



## Lab 3

Section 1, CMPEN 331

sns5787

## Images:

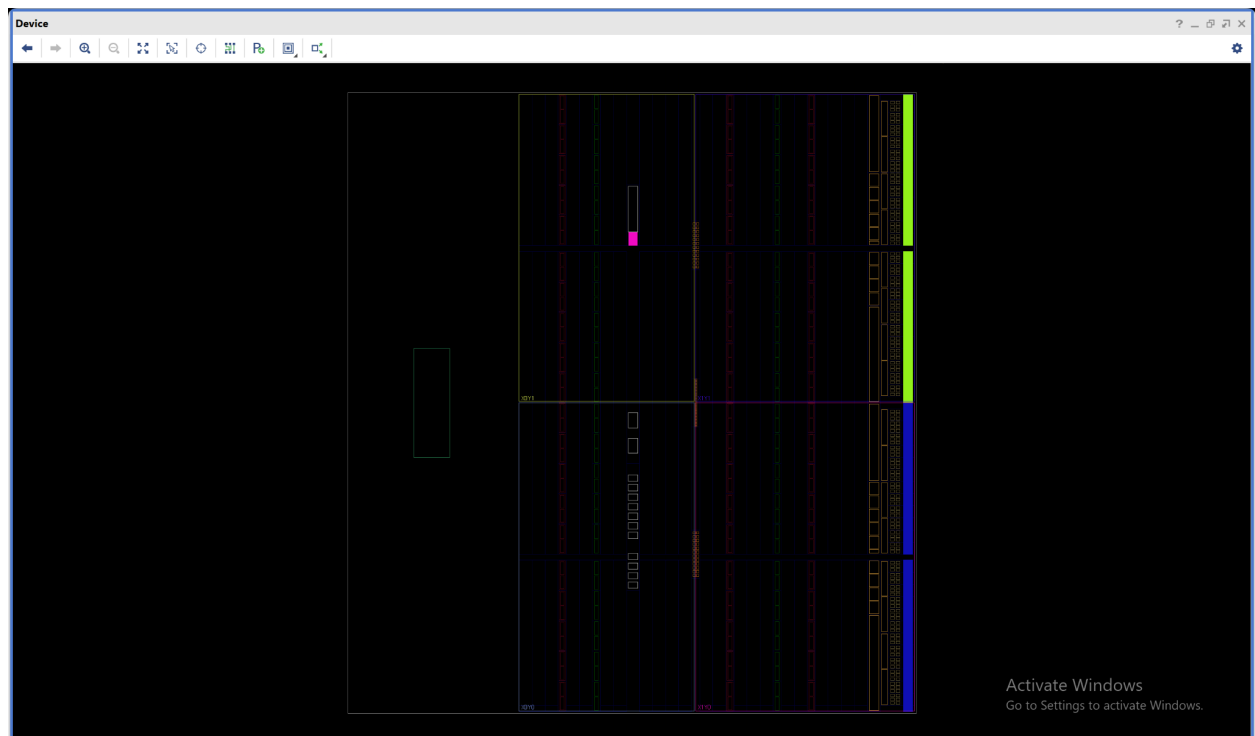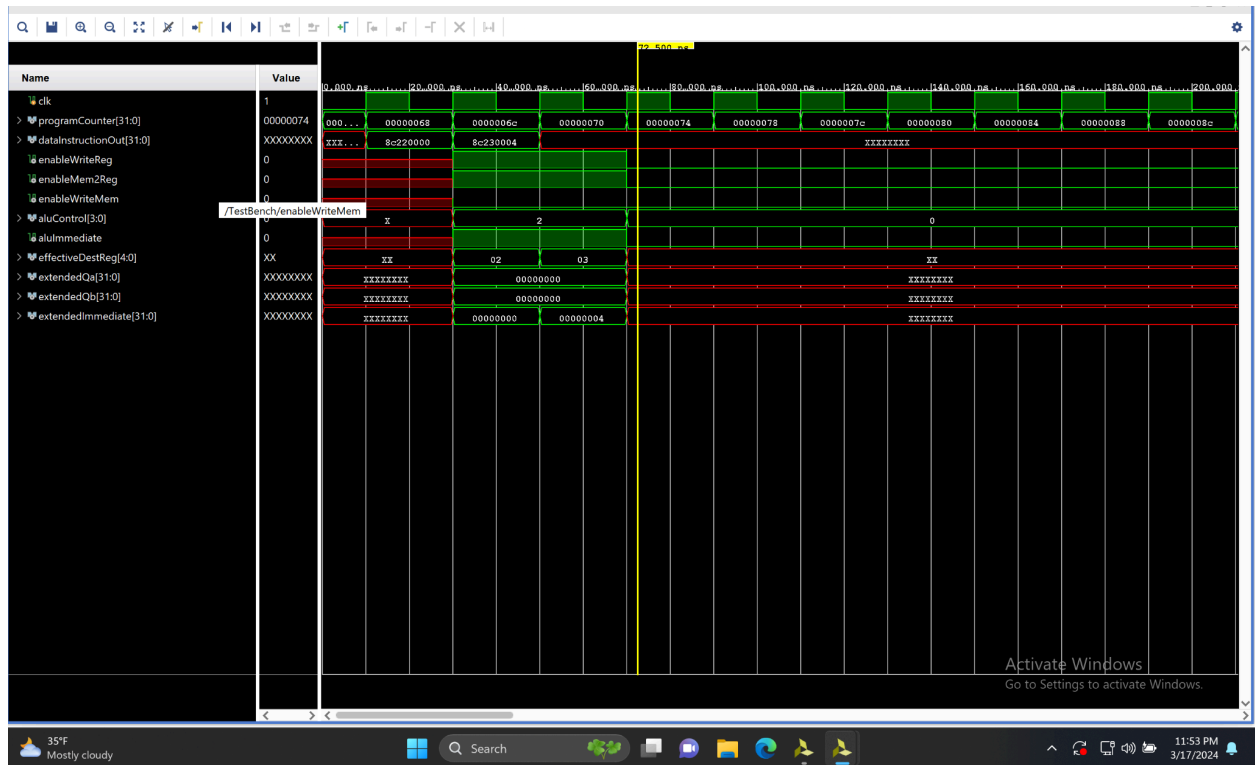

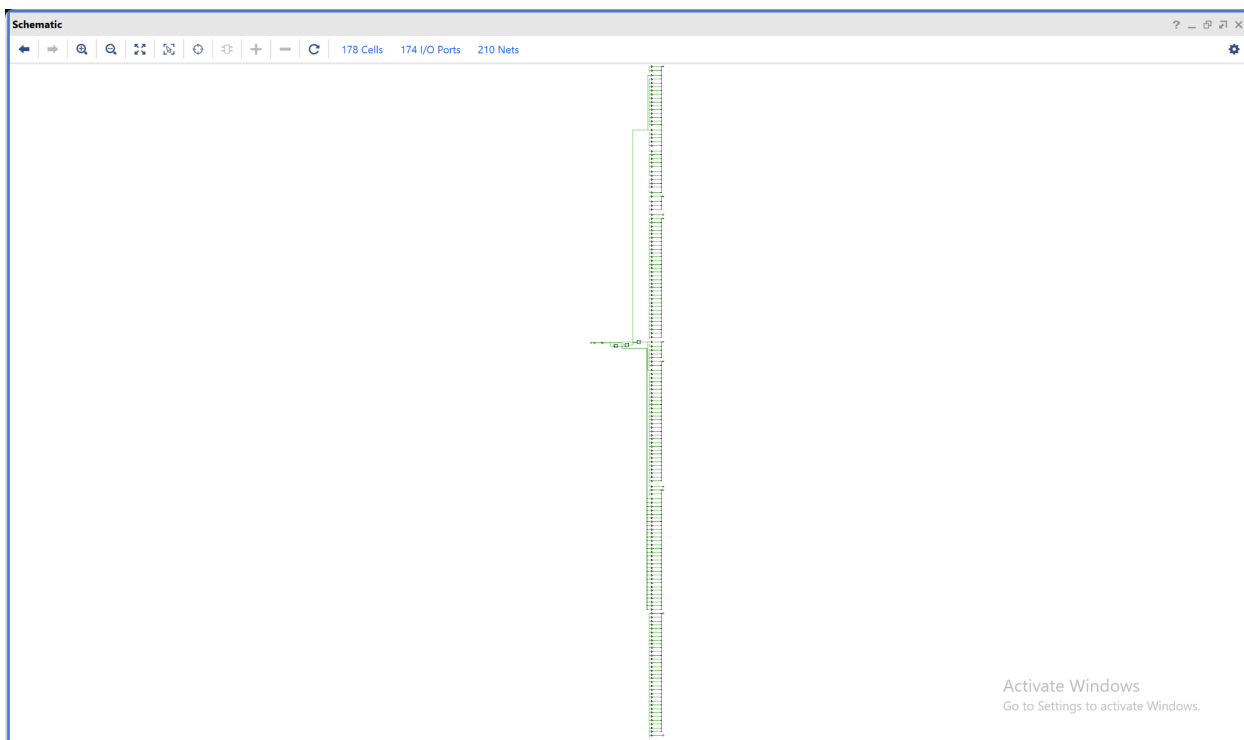 

## Datapath Code:

```
module Datapath(  
    input clk,  
    output wire [31:0] programCounter,  
    output wire [31:0] dataInstructionOut,  
    output wire enableWriteReg,  
    output wire enableMem2Reg,  
    output wire enableWriteMem,  
    output wire [3:0] aluControl,  
    output wire aluImmediate,  
    output wire [4:0] effectiveDestReg,  
    output wire [31:0] extendedQa,  
    output wire [31:0] extendedQb,  
    output wire [31:0] extendedImmediate  
);  
  
    wire writeRegEnable;  
    wire mem2RegEnable;  
    wire writeMemEnable;  
    wire aluImmediateCalc;  
    wire regRt;  
    wire [4:0] destinationReg;  
    wire [31:0] extendedA;
```

```

wire [31:0] extendedB;

wire [31:0] immediate32;

wire [31:0] nextProgramCounter;

wire [31:0] instructionOut;

wire [3:0] aluCtrl;

wire [15:0] immediate;

wire [4:0] sourceRs;

wire [4:0] targetRt;

wire [4:0] destinationRd;

wire [5:0] opcode;

wire [5:0] functionCode;

```

```

ProgramCounter ProgramCounter(.clk(clk), .nextPc(nextProgramCounter),
.pc(programCounter));

pcAdder pcAdder_db(.pc(programCounter), .nextPc(nextProgramCounter));

InstructionMemory InstructionMemory_db(.pc(programCounter),
.instOut(instructionOut));

IFIDpipelineReg IFIDpipelineReg_db(.clk(clk), .instOut(instructionOut),
.dinstOut(dataInstructionOut));

ControlUnit controlUnit_db(.op(opcode), .func(functionCode), .wreg(writeRegEnable),
.m2reg(mem2RegEnable), .wmem(writeMemEnable), .aluc(aluCtrl),
.aluimm(aluImmediateCalc), .regrt(regRt));

```

```
    RegrtMultiplexer RegrtMultiplexer_db(.rt(targetRt), .rd(destinationRd), .regrt(regRt),  
.destReg(destinationReg));
```

```
    RegisterFile RegisterFile_db(.rs(sourceRs), .rt(targetRt), .qa(extendedA),  
.qb(extendedB));
```

```
    ImmediateExtender ImmediateExtender_db(.imm(immediate),  
.imm32(immediate32));
```

```
    IDXEPipeline IDXEPipeline_db(  
    .wreg(writeRegEnable),  
    .m2reg(mem2RegEnable),  
    .wmem(writeMemEnable),  
    .aluc(aluCtrl),  
    .aluimm(aluImmediateCalc),  
    .destReg(destinationReg),  
    .qa(extendedA),  
    .qb(extendedB),  
    .imm32(immediate32),  
    .clk(clk),  
    .ewreg(enableWriteReg),  
    .em2reg(enableMem2Reg),  
    .ewmem(enableWriteMem),  
    .ealuc(aluControl),  
    .ealuimm(aluImmediate),  
    .edestReg(effectiveDestReg),
```

```

        .eqa(extendedQa),
        .eqb(extendedQb),
        .eimm32(extendedImmediate)
    );

```

```

    assign opcode = dataInstructionOut[31:26];
    assign functionCode = dataInstructionOut[5:0];
    assign sourceRs = dataInstructionOut[25:21];
    assign targetRt = dataInstructionOut[20:16];
    assign destinationRd = dataInstructionOut[15:11];
    assign immediate = dataInstructionOut[15:0];

```

```

module ProgramCounter( //PC pipeline
    input clk,
    input [31:0] nextPc,
    output reg [31:0] pc
);

```

```

initial
begin
    pc = 32'd100; //set

```

end

always @(posedge clk) //update

begin

pc = nextPc;

end

endmodule

module pcAdder(

input [31:0] pc,

output reg [31:0] nextPc

);

always @(\*) begin

nextPc = pc + 32'b00000000000000000000000000000000100;

end

endmodule



```

module InstructionMemory(
    input [31:0] pc,
    output reg [31:0] instOut
);
    reg [31:0] memory [0:63]; //32x64

    initial begin
        memory[25] = {6'b100011, 5'b00001, 5'b00010, 5'b00000, 5'b00000, 6'b000000};
//lw $v0, 00($at

        memory[26] = {6'b100011, 5'b00001, 5'b00011, 5'b00000, 5'b00000, 6'b000100};
//lw $v1, 04($at

        end

    always @ (*)
        begin
            instOut = memory[pc[7:2]];

        end
endmodule

```

```

module IFIDpipelineReg(
    input clk,

```

```
input [31:0] instOut,  
output reg [31:0] dinstOut  
);
```

```
always @ (posedge clk)  
begin  
    dinstOut = instOut;  
end
```

Endmodule

```
module ControlUnit(  
    input [5:0] op,  
    input [5:0] func,  
  
    output reg wreg,  
    output reg m2reg,  
    output reg wmem,  
    output reg [3:0] aluc,  
    output reg aluimm,  
    output reg regrt  
);
```

```
// Continuously update control signals based on decoded instruction
```

```
always @ (*) begin
```

```
// Decode instruction opcode
```

```
case (op)
```

```
// R-type instructions
```

```
6'b000000: begin
```

```
// Decode R-type function code
```

```
case (func)
```

```
// ADD instruction
```

```
6'b100000: begin
```

```
// Set control signals for ADD:
```

```
// - Write result to register file
```

```
// - No memory access
```

```
// - Use ALU for addition
```

```
// - Source operands from registers
```

```
// - Destination register address is second source (rs2)
```

```
wreg = 1'b1;
```

```
m2reg = 1'b0;
```

```
wmem = 1'b0;
```

```
aluc = 4'b0010; // ALU operation for addition
```

```

    aluimm = 1'b0;

    regrt = 1'b0;

end

// Default behavior for unspecified R-type functions
default: begin

    // Set default control signals (e.g., all signals to 0)

    // for unspecified R-type instructions

    wreg = 1'b0;

    m2reg = 1'b0;

    wmem = 1'b0;

    aluc = 4'b0000;

    aluimm = 1'b0;

    regrt = 1'b0;

end

endcase

end

// LW instruction (load word from memory)
6'b100011: begin

    // Set control signals for LW:

    // - Write result to register file

    // - Read data from memory

```

```
// - No memory write

// - Use ALU for address calculation (addition)

// - ALU source from registers and immediate

// - Destination register address is third source (rt)

wreg = 1'b1;

m2reg = 1'b1;

wmem = 1'b0;

aluc = 4'b0010; // ALU operation for addition

aluimm = 1'b1;

regrt = 1'b1;

end
```

```
// Default behavior for unspecified opcodes

default: begin

// Set default control signals (e.g., all signals to 0)

// for unspecified instructions

wreg = 1'b0;

m2reg = 1'b0;

wmem = 1'b0;

aluc = 4'b0000;

aluimm = 1'b0;

regrt = 1'b0;

end
```

```
        endcase
    end

    module RegrtMultiplexer(
        input [4:0] rt,
        input [4:0] rd,
        input regrt,
        output reg [4:0] destReg
    );
```

```
        always @(*)
        begin
            if (regrt == 0)
                destReg = rd;
            else
                destReg = rt;
        end
    endmodule
```

```
    module RegisterFile(
        //inputs
        input [4:0] rs,
        input [4:0] rt,
```

```
//outputs
```

```
output reg [31:0] qa,
```

```
output reg [31:0] qb
```

```
);
```

```
reg [31:0] register [0:31]; //32x32
```

```
integer r;
```

```
initial begin
```

```
    for (r = 0; r <= 31; r = r + 1) begin
```

```
        register[r] = 0; //init all to 0
```

```
    end
```

```
end
```

```
always @ (*)
```

```
begin //block updates
```

```
    qa = register[rs];
```

```
    qb = register[rt];
```

```
end
```

```
endmodule
```

```

module ImmediateExtender(
    input [15:0] imm,
    output reg [31:0] imm32
);

always @ (*)
    begin
        imm32 = {{16{imm[15]}}, imm};
    end
endmodule

```

```

module IDEXEPipeline(
    input wreg,
    input m2reg,
    input wmem,
    input [3:0] aluc,
    input aluimm,
    input [4:0] destReg,
    input [31:0] qa,
    input [31:0] qb,
    input [31:0] imm32,
    input clk,

```



```
output reg ewreg,  
output reg em2reg,  
output reg ewmem,  
output reg [3:0] ealuc,  
output reg ealuimm,  
output reg [4:0] edestReg,  
output reg [31:0] eqa,  
output reg [31:0] eqb,  
output reg [31:0] eimm32  
);
```

```
always @ (posedge clk)  
begin  
    ewreg = wreg;  
    em2reg = m2reg;  
    ewmem = wmem;  
    ealuc = aluc;  
    ealuimm = aluimm;  
    edestReg = destReg;  
    eqa = qa;  
    eqb = qb;  
    eimm32 = imm32;
```

```
        end  
Endmodule
```

### **Workbench Code:**

```
module TestBench;  
  
    reg clk;  
  
    wire [31:0] programCounter;  
    wire [31:0] dataInstructionOut;  
    wire enableWriteReg;  
    wire enableMem2Reg;  
    wire enableWriteMem;  
    wire [3:0] aluControl;  
    wire aluImmediate;  
    wire [4:0] effectiveDestReg;  
    wire [31:0] extendedQa;  
    wire [31:0] extendedQb;  
    wire [31:0] extendedImmediate;
```

```
initial begin
```

```
    clk <= 1'b0;
```

```
end
```

```
Datapath datapath(
```

```
    .clk(clk),
```

```
    .programCounter(programCounter),
```

```
    .dataInstructionOut(dataInstructionOut),
```

```
    .enableWriteReg(enableWriteReg),
```

```
    .enableMem2Reg(enableMem2Reg),
```

```
    .enableWriteMem(enableWriteMem),
```

```
    .aluControl(aluControl),
```

```
    .aluImmediate(aluImmediate),
```

```
    .effectiveDestReg(effectiveDestReg),
```

```
    .extendedQa(extendedQa),
```

```
    .extendedQb(extendedQb),
```

```
    .extendedImmediate(extendedImmediate)
```

```
);
```

```
always begin
```

```
    #10;
```

```
    clk = ~clk;
```

end

endmodule