

Sethu Senthil


Lab 4

Section 1, CMPEN 331


sns5787



Images:


Lab 3 Waveform:

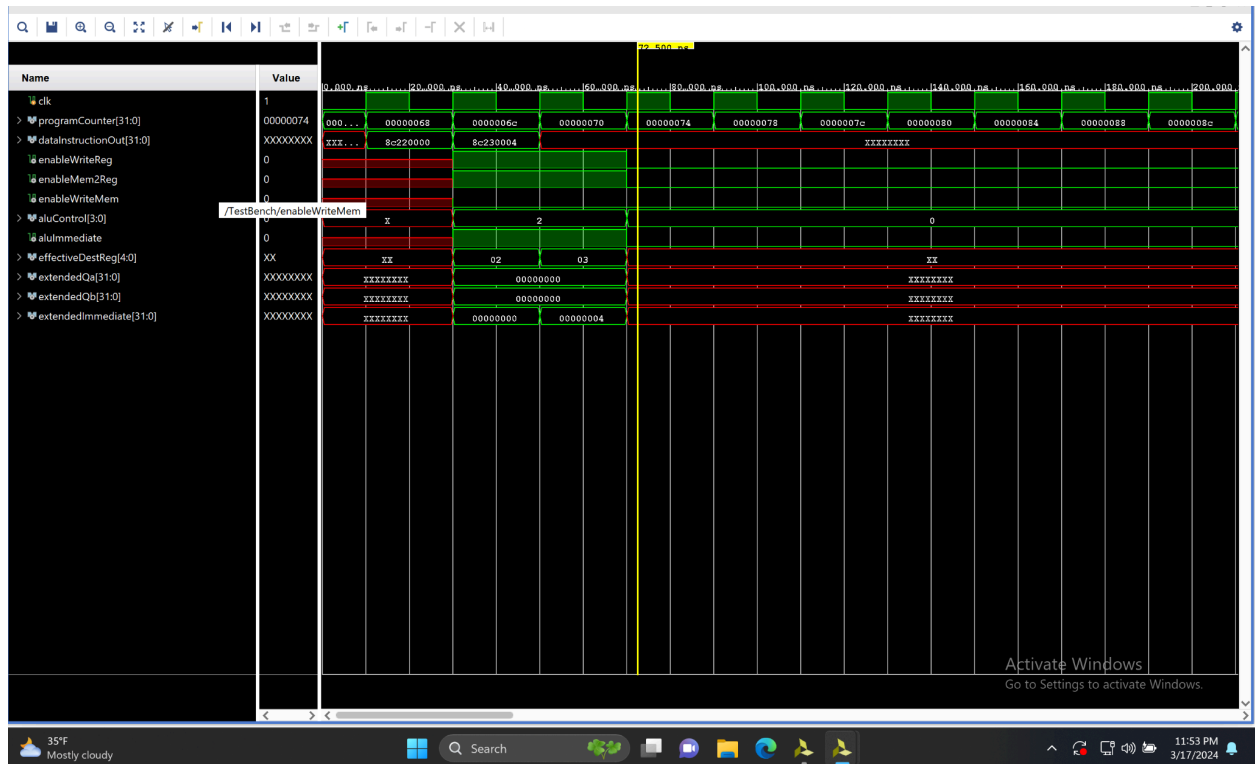

Lab 4 Waveform:

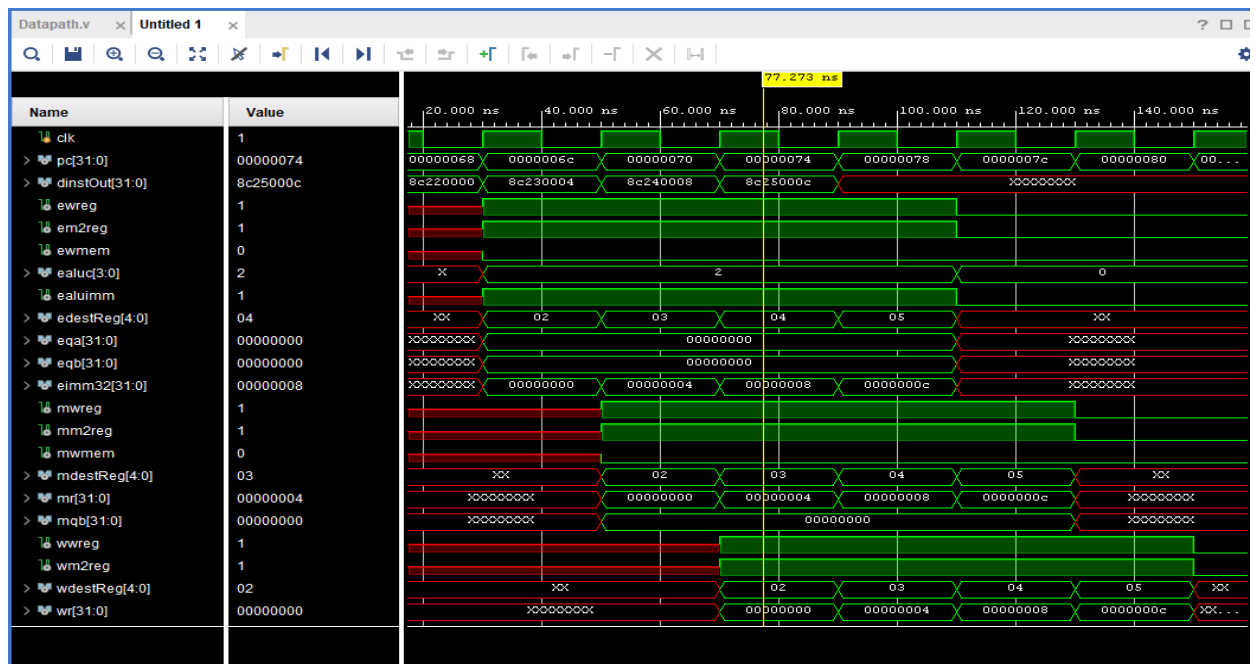

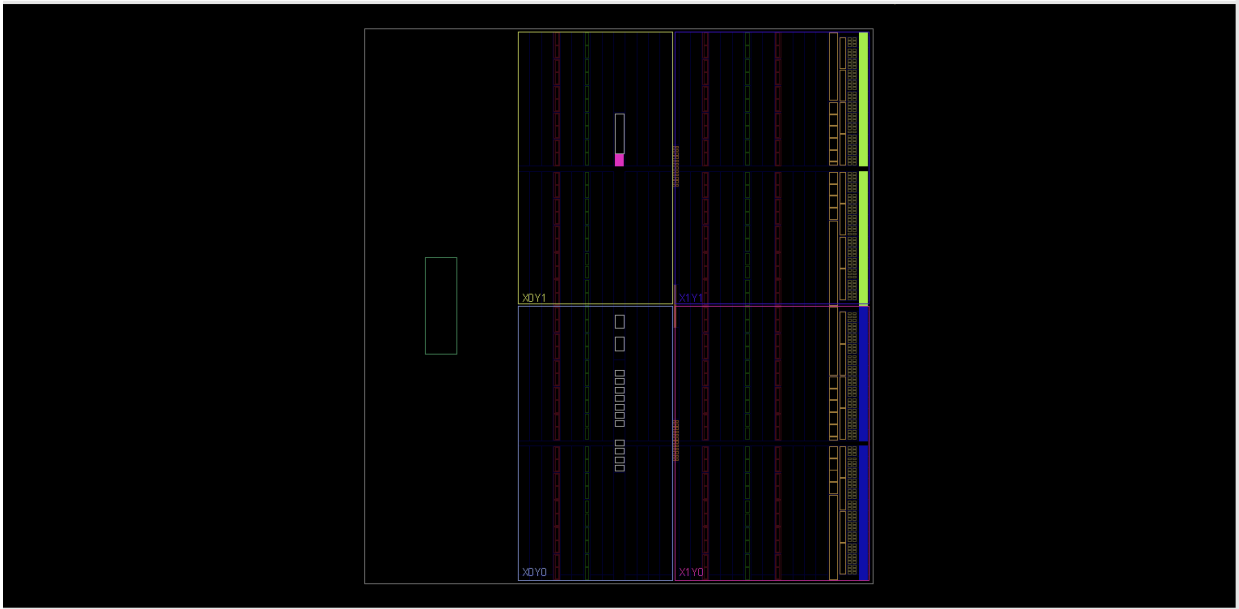 

 

Datapath Code:

```
`timescale 1ns / 1ps
```

```
////////////////////////////////////////////////////////////////
```

```
// Company:
```

```
// Engineer:
```

```
//
```

```
// Create Date: 04/07/2024 09:24:34 PM
```

```
// Design Name:
```

```
// Module Name: Datapath
```

```
// Project Name:
```

```
// Target Devices:
```

// Tool Versions:

// Description:

//

// Dependencies:

//

// Revision:

// Revision 0.01 - File Created

// Additional Comments:

//

//

module Datapath(

 // Lab 3 ----- IDEXEpipeline

 input clk, // Clock signal

 output wire [31:0] pc, // Program Counter

 output wire [31:0] dinstOut, // Data from the Instruction Memory

 output wire ewreg, // Control signal for write enable in the EX stage

 output wire em2reg, // Control signal for write enable in the Memory stage

 output wire ewmem, // Control signal for write enable in the MEM stage

 output wire [3:0] ealuc, // ALU control signal in the EX stage

 output wire ealuimm, // ALU immediate in the EX stage

 output wire [4:0] edestReg, // Destination register address in the EX stage

 output wire [31:0] eqa, // Data from source register A in the EX stage

 output wire [31:0] eqb, // Data from source register B in the EX stage

```
output wire [31:0] eimm32 // 32-bit immediate in the EX stage
```

```
// Lab 4 ----- EXEMEM
```

```
,output wire mwreg,      // Control signal for write enable in the MEM stage
output wire mm2reg,      // Control signal for write enable in the M2 stage (MEM-WB)
output wire mwmem,       // Control signal for memory write enable in the MEM stage
output wire [4:0] mdestReg, // Destination register address in the MEM stage
output wire [31:0] mr,    // Data read from memory in the MEM stage
output wire [31:0] mqb    // Data from source register B in the MEM stage
```

```
// Lab 4 ----- MEMWB
```

```
,output wire wwreg,      // Control signal for write enable in the WB stage
output wire wm2reg,      // Control signal for write enable in the M2 stage (WB)
output wire [4:0] wdestReg, // Destination register address in the WB stage
output wire [31:0] wr,    // Result to be written to the register file in the WB stage
output wire [31:0] wdo    // Data read from memory or ALU result to be written to the
register file
```

```
);
```

```
// Lab 3 ----- wires
```

```
wire wreg;          // Control signal for write enable
wire m2reg;         // Control signal for write enable (Memory stage)
wire wmem;          // Control signal for memory write enable
```

```

wire aluimm;          // ALU immediate value

wire regrt;          // Control signal for selecting a register

wire [4:0] destReg;   // Destination register address

wire [31:0] qa;       // Data from source register A

wire [31:0] qb;       // Data from source register B

wire [31:0] imm32;    // 32-bit immediate value

wire [31:0] nextPc;   // Next program counter value

wire [31:0] instOut;  // Data from the Instruction Memory

wire [3:0] aluc;      // ALU control signal

wire [15:0] imm;      // Immediate value

wire [4:0] rs;        // Source register address

wire [4:0] rt;        // Source register address

wire [4:0] rd;        // Destination register address

wire [5:0] op;        // Operation code

wire [5:0] func;      // Function code


// Lab 4 ----- wires

wire [31:0] b;        // Data input to the ALU

wire [31:0] r;        // Result from the ALU

wire [31:0] mdo;      // Data read from memory or result from ALU


//connect components

```

```

ProgramCounter IF_ProgramCounter_datapath(.clk(clk), .nextPc(nextPc), .pc(pc));

pcAdder IF_pcAdder_datapath(.pc(pc), .nextPc(nextPc));

InstructionMemory IF_InstructionMemory_dp(.pc(pc), .instOut(instOut));

IFIDpipelineReg IFIDpipelineReg_datapath(.clk(clk), .instOut(instOut),
.dinstOut(dinstOut));

ControlUnit ID_controlUnit_datapath(.op(op), .func(func), .wreg(wreg),
.m2reg(m2reg), .wmem(wmem), .aluc(aluc), .aluimm(aluimm), .regrt(regrt));

RegrtMultiplexer ID_RegrtMultiplexer_datapath(.rt(rt), .rd(rd), .regrt(regrt),
.destReg(destReg));

RegisterFile ID_RegisterFile_datapath(.rs(rs), .rt(rt), .qa(qa), .qb(qb));

ImmediateExtender ID_ImmediateExtender_datapath(.imm(imm), .imm32(imm32));

IDEXEpipeline IDEXEpipeline_datapath(
    .wreg(wreg),
    .m2reg(m2reg),
    .wmem(wmem),
    .aluc(aluc),
    .aluimm(aluimm),
    .destReg(destReg),
    .qa(qa),
    .qb(qb),
    .imm32(imm32),
    .clk(clk),
    .ewreg(ewreg),

```



```
.em2reg(em2reg),  
.ewmem(ewmem),  
.ealuc(ealuc),  
.ealuimm(ealuimm),  
.edestReg(edestReg),  
.eqa(eqa),  
.eqb(eqb),  
.eimm32(eimm32)  
);
```

```
ALU EXE_ALU_datapath(.eqa(eqa), .b(b), .ealuc(ealuc), .r(r));
```

```
ALUMux EXE_ALUMux_datapath(.eqb(eqb), .eimm32(eimm32), .ealuimm(ealuimm),  
.b(b));
```

```
EXEMEMpipeline EXEMempipeline_datapath(
```

```
.ewreg(ewreg),  
.em2reg(em2reg),  
.ewmem(ewmem),  
.edestReg(edestReg),  
.r(r),  
.eqb(eqb),  
.clk(clk),  
.mwreg(mwreg),  
.mm2reg(mm2reg),
```

```
.mwmem(mwmem),  
.mdestReg(mdestReg),  
.mr(mr),  
.mqb(mqb)  
);  
DataMemory MEM_DataMemory_datapath(.mr(mr), .mqb(mqb), .mwmem(mwmem),  
.clk(clk), .mdo(mdo));
```

```
MEMWBpipeline MEMWBpipeline_datapath(
```

```
.mwreg(mwreg),  
.mm2reg(mm2reg),  
.mdestReg(mdestReg),  
.mr(mr),  
.mdo(mdo),  
.clk(clk),  
.wwreg(wwreg),  
.wm2reg(wm2reg),  
.wdestReg(wdestReg),  
.wr(wr),  
.wdo(wdo)  
);
```

```
    assign op = dinstOut[31:26];

    assign func = dinstOut[5:0];

    assign rs = dinstOut[25:21];

    assign rt = dinstOut[20:16];

    assign rd = dinstOut[15:11];

    assign imm = dinstOut[15:0];

endmodule


`timescale 1ns / 1ps

////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////

// Company:

// Engineer:

//

// Create Date: 04/07/2024 09:31:23 PM

// Design Name:

// Module Name: IF_ProgramCounter_dp

// Project Name:

// Target Devices:

// Tool Versions:

// Description:

//

// Dependencies:

//
```

```
// Revision:
```

```
// Revision 0.01 - File Created
```

```
// Additional Comments:
```

```
//
```

```
////////////////////////////////////////////////////////////////
```

```
module ProgramCounter(
```

```
    input clk,          // Input for clock signal, triggering positive edge updates.
```

```
    input [31:0] nextPc, // Input representing the next program counter value.
```

```
    output reg [31:0] pc // Output representing the current program counter value.
```

```
);
```

```
initial
```

```
begin
```

```
    pc = 32'd100;    // Initializing the program counter to start at 100.
```

```
end
```

```
always @(posedge clk)
```

```
begin
```

```
    pc = nextPc;    // Updating the program counter on the positive clock edge.
```

```
end
```

endmodule

```
`timescale 1ns / 1ps
```

////////////////////////////////////

```
// Company:
```

```
// Engineer:
```

//

```
// Create Date: 04/07/2024 09:32:38 PM
```

```
// Design Name:
```

```
// Module Name: IF_pcAdder_dp
```

```
// Project Name:
```

```
// Target Devices:
```

```
// Tool Versions:
```

```
// Description:
```

//

```
// Dependencies:
```

//

```
// Revision:
```

```
// Revision 0.01 - File Created
```

// Additional Comments:

//

////////////////////////////////////

```

module pcAdder( // Module defining the program counter adder for CPU operation.
    input [31:0] pc, // Input representing the current program counter, 32 bits wide.
    output reg [31:0] nextPc // Output register representing the next program counter,
    also 32 bits wide.
);

    always @(*) begin // Continuous updating of nextPc whenever any input signal
changes.
        nextPc <= pc + 32'b00000000000000000000000000000000100; // Updating nextPc by
adding 4 to the input program counter.
    end // End of always block

endmodule

`timescale 1ns / 1ps

////////////////////////////////////

// Company:

// Engineer:

//

// Create Date: 04/07/2024 09:43:21 PM

// Design Name:

// Module Name: IF_InstructionMemory_dp

```

```
// Project Name:

// Target Devices:

// Tool Versions:

// Description:

//

// Dependencies:

//

// Revision:

// Revision 0.01 - File Created

// Additional Comments:

//

////////////////////////////////////////////////////////////////
```

```
module InstructionMemory( // Module defining the instruction memory component within
the CPU.
```

```
    input [31:0] pc, // Input representing the program counter.
```

```
    output reg [31:0] instOut // Output representing the instruction fetched from memory.
```

```
);
```

```
    reg [31:0] memory [0:63]; // 32x64 array used to store instructions in memory.
```

```
    initial begin
```

```
        // Initializing memory with instructions
```

```

// lw $v0, 00($at)

memory[25] = {6'b100011, 5'b00001, 5'b00010, 5'b00000, 5'b00000, 6'b000000};

// lw $v1, 04($at)

memory[26] = {6'b100011, 5'b00001, 5'b00011, 5'b00000, 5'b00000, 6'b000100};

// lw $a0, 08($at)

memory[27] = {6'b100011, 5'b00001, 5'b00100, 5'b00000, 5'b00000, 6'b001000};

// lw $a1, 12($at)

memory[28] = {6'b100011, 5'b00001, 5'b00101, 5'b00000, 5'b00000, 6'b001100};

end

```

always @ (*) // Continuous updating of instruction output based on the program counter bits 7 to 2.

```

begin

    instOut <= memory[pc[7:2]];

end

endmodule

```

```
`timescale 1ns / 1ps
```

```
////////////////////////////////////////////////////////////////
```

```
// Company:
```

```
// Engineer:
```

```
//
```

```
// Create Date: 04/07/2024 09:46:22 PM
```



```
// Design Name:

// Module Name: IFIDpipelineReg_dp

// Project Name:

// Target Devices:

// Tool Versions:

// Description:

//

// Dependencies:

//

// Revision:

// Revision 0.01 - File Created

// Additional Comments:

//

////////////////////////////////////////////////////////////////
```

```
module IFIDpipelineReg( //IFID pipeline

    input clk, //clock input needed as dinstOut only updates on the positive edge of clock.

    input [31:0] instOut, //input

    output reg [31:0] dinstOut //output

);
```

always @ (posedge clk) //always block that will only update dinstOut on the positive edge of the clock. dinstOut is to the instOut input of this module.

```
begin
    dinstOut <= instOut;
end
```

endmodule

```
`timescale 1ns / 1ps
```

```
////////////////////////////////////////////////////////////////
```

```
// Company:
```

```
// Engineer:
```

```
//
```

```
// Create Date: 04/07/2024 09:48:40 PM
```

```
// Design Name:
```

```
// Module Name: ID_controlUnit_dp
```

```
// Project Name:
```

```
// Target Devices:
```

```
// Tool Versions:
```

```
// Description:
```

```
//
```

```
// Dependencies:
```

```
//
```

// Revision:

// Revision 0.01 - File Created

// Additional Comments:

//

//

module ControlUnit(// Module defining the control unit of the CPU.

// Inputs

input [5:0] op, // Opcode input.

input [5:0] func, // Function input.

// Outputs

output reg wreg, // Write to register file.

output reg m2reg, // Memory to register.

output reg wmem, // Write to memory.

output reg [3:0] aluc, // ALU control.

output reg aluimm, // ALU immediate source.

output reg regrt // Destination register address.

);

always @ (*) begin // Continuous updating of control signals based on op and func values.

```

case (op) // Checking the opcode portion.

6'b000000: // R-type instructions

begin

    case (func) // Checking specific function values.

        6'b100000: // ADD instruction

        begin

            // Setting control signals for ADD instruction

            wreg = 1'b1; // Write to the register file

            m2reg = 1'b0; // Do not write to memory

            wmem = 1'b0; // Do not write to memory

            aluc = 4'b0010; // ALU operation for addition

            aluimm = 1'b0; // ALU source from registers

            regrt = 1'b0; // Destination register address

        end

    default: // Default behavior for unspecified func values

    begin

        // Set default control signals here

        // For example, you can set all signals to 0.

        wreg = 1'b0;

        m2reg = 1'b0;

        wmem = 1'b0;

        aluc = 4'b0000;

```

```
        aluimm = 1'b0;

        regrt = 1'b0;

    end

endcase

end
```

```
6'b100011: // LW instruction
```

```
begin

    // Setting control signals for LW instruction

    wreg = 1'b1; // Write to the register file

    m2reg = 1'b1; // Write to memory

    wmem = 1'b0; // Do not write to memory

    aluc = 4'b0010; // ALU operation for addition

    aluimm = 1'b1; // ALU source from registers

    regrt = 1'b1; // Destination register address

end
```

```
default: // Default behavior for unspecified op values
```

```
begin

    // Set default control signals here for unspecified op values

    // For example, you can set all signals to 0.

    wreg = 1'b0;

    m2reg = 1'b0;
```

```
wmem = 1'b0;

aluc = 4'b0000;

aluimm = 1'b0;

regrt = 1'b0;

end

endcase

end

endmodule


`timescale 1ns / 1ps

////////////////////////////////////////////////////////////////

// Company:

// Engineer:

//

// Create Date: 04/07/2024 09:50:07 PM

// Design Name:

// Module Name: ID_RegrtMultiplexer_dp

// Project Name:

// Target Devices:

// Tool Versions:

// Description:

//
```

```
// Dependencies:
```

```
//
```

```
// Revision:
```

```
// Revision 0.01 - File Created
```

```
// Additional Comments:
```

```
//
```

```
////////////////////////////////////////////////////////////////
```

```
module RegrtMultiplexer(
```

```
    // Inputs
```

```
    input [4:0] rt,    // Input register value rt
```

```
    input [4:0] rd,    // Input register value rd
```

```
    input regrt,      // Control signal to select the output (0 for rd, 1 for rt)
```

```
    // Output
```

```
    output reg [4:0] destReg // Output register value (selected based on the control  
signal)
```

```
);
```

```
always @(*)
```

```
begin
```

```
    if (regrt == 0)
```

```
        destReg = rd;  // Select rd as the output when regrt is 0.
    else
        destReg = rt;  // Select rt as the output when regrt is 1.
    end
```

```
endmodule
```

```
`timescale 1ns / 1ps
```

```
////////////////////////////////////////////////////////////////
```

```
// Company:
```

```
// Engineer:
```

```
//
```

```
// Create Date: 04/07/2024 09:54:38 PM
```

```
// Design Name:
```

```
// Module Name: ID_RegisterFile_dp
```

```
// Project Name:
```

```
// Target Devices:
```

```
// Tool Versions:
```

```
// Description:
```

```
//
```

```
// Dependencies:
```

```
//
```

```
// Revision:
```



```
// Revision 0.01 - File Created
```

```
// Additional Comments:
```

```
//
```

```
////////////////////////////////////////////////////////////////
```

```
module RegisterFile(
```

```
    // Inputs
```

```
    input [4:0] rs,    // Input for the source register (rs)
```

```
    input [4:0] rt,    // Input for the target register (rt)
```

```
    // Outputs
```

```
    output reg [31:0] qa, // Output for the value stored in the source register
```

```
    output reg [31:0] qb // Output for the value stored in the target register
```

```
);
```

```
reg [31:0] register [0:31]; // 32x32 array for registers (register file)
```

```
// Initialize all registers to 0
```

```
integer r;
```

```
initial begin
```

```
    for (r = 0; r <= 31; r = r + 1) begin
```

```
        register[r] = 0; // Initialize each register to 0.
```

```

        end

end

always @ (*) // Continuous updating of qa and qb based on rs and rt inputs.

begin

    qa = register[rs]; // Output qa corresponds to the value stored in the source register
(rs).

    qb = register[rt]; // Output qb corresponds to the value stored in the target register
(rt).

end

endmodule


`timescale 1ns / 1ps

////////////////////////////////////

// Company:

// Engineer:

//

// Create Date: 04/07/2024 09:56:22 PM

// Design Name:

// Module Name: ID_ImmediateExtender_dp

// Project Name:

// Target Devices:

```

// Tool Versions:

// Description:

//

// Dependencies:

//

// Revision:

// Revision 0.01 - File Created

// Additional Comments:

//

//

module ImmediateExtender(// Module for immediate value extension.

input [15:0] imm, // Input immediate value.

output reg [31:0] imm32 // Output extended immediate value.

);

always @ (*) // Continuous update of imm32 value.

begin

imm32 = {{16{imm[15]}}, imm}; // Sign extension: Replicating the sign bit to fill

the upper 16 bits.

end

endmodule

```
`timescale 1ns / 1ps
```

```
////////////////////////////////////////////////////////////////
```

```
// Company:
```

```
// Engineer:
```

```
//
```

```
// Create Date: 04/07/2024 09:57:11 PM
```

```
// Design Name:
```

```
// Module Name: IDEXEpipeline_dp
```

```
// Project Name:
```

```
// Target Devices:
```

```
// Tool Versions:
```

```
// Description:
```

```
//
```

```
// Dependencies:
```

```
//
```

```
// Revision:
```

```
// Revision 0.01 - File Created
```

```
// Additional Comments:
```

```
//
```

```
////////////////////////////////////////////////////////////////
```

```
module IDEXEpipeline(
```

// Inputs

```
input wreg,          // Control signal for write enable to the register file
input m2reg,         // Control signal for write enable to the register file (M2 stage)
input wmem,          // Control signal for memory write enable
input [3:0] aluc,    // ALU control signal
input aluimm,        // ALU immediate value
input [4:0] destReg, // Destination register address
input [31:0] qa,     // Value from source register A
input [31:0] qb,     // Value from source register B
input [31:0] imm32,  // 32-bit immediate value
input clk,           // Clock signal
```

// Outputs

```
output reg ewreg,    // Output for write enable signal
output reg em2reg,   // Output for write enable signal (M2 stage)
output reg ewmem,    // Output for memory write enable signal
output reg [3:0] ealuc, // Output for ALU control signal
output reg ealuimm,  // Output for ALU immediate value
output reg [4:0] edestReg, // Output for destination register address
output reg [31:0] eqa, // Output for source register A value
output reg [31:0] eqb, // Output for source register B value
output reg [31:0] eimm32 // Output for 32-bit immediate value
```

);

```

// On the positive edge of the clock, update the output signals with the input values.
always @ (posedge clk)

begin

    ewreg = wreg;    // Update write enable signal for register file writing.

    em2reg = m2reg;  // Update write enable signal for register file writing in M2 stage.

    ewmem = wmem;    // Update memory write enable signal.

    ealuc = aluc;    // Update ALU control signal.

    ealuimm = aluimm; // Update ALU immediate value.

    edestReg = destReg; // Update destination register address.

    eqa = qa;        // Update source register A value.

    eqb = qb;        // Update source register B value.

    eimm32 = imm32;  // Update 32-bit immediate value.

end

endmodule


`timescale 1ns / 1ps

/////////////////////////////////////////////////////////////////

// Company:

// Engineer:

//

// Create Date: 04/07/2024 10:04:27 PM

```

```
// Design Name:
// Module Name: EXE_ALU_dp
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
////////////////////////////////////
```

```
module ALU(
    input [31:0] eqa,    // Input A for the ALU
    input [31:0] b,      // Input B for the ALU
    input [3:0] ealuc,   // ALU control signal
    output reg [31:0] r  // Output of the ALU
);
```

```
// ALU operation codes

// 0000 - AND

// 0001 - OR

// 0010 - ADD

// 0110 - SUBTRACT

// 0111 - SET LESS THAN

// 1100 - NOR

// 1111 - XOR
```

```
always @ (*)
```

```
begin
```

```
    case(ealuc)
```

```
        4'b0000: // AND
```

```
            begin
```

```
                r = eqa & b; // Perform AND operation between eqa and b.
```

```
            end
```

```
        4'b0001: // OR
```

```
            begin
```

```
                r = eqa | b; // Perform OR operation between eqa and b.
```

```
            end
```

```
        4'b0010: // ADD
```



```
begin
```

```
    r = eqa + b; // Perform ADD operation between eqa and b.
```

```
end
```

```
4'b0110: // SUBTRACT
```

```
begin
```

```
    r = eqa - b; // Perform SUBTRACT operation between eqa and b.
```

```
end
```

```
4'b1100: // NOR
```

```
begin
```

```
    r = ~(eqa | b); // Perform NOR operation between eqa and b.
```

```
end
```

```
4'b1111: // XOR
```

```
begin
```

```
    r = eqa ^ b; // Perform XOR operation between eqa and b.
```

```
end
```

```
endcase
```

```
end
```

```
endmodule
```

```
`timescale 1ns / 1ps
```

////////////////////////////////////

```
// Company:
```

```
// Engineer:
```

//

```
// Create Date: 04/07/2024 10:06:38 PM
```

```
// Design Name:
```

```
// Module Name: EXE_ALUMux_dp
```

```
// Project Name:
```

```
// Target Devices:
```

```
// Tool Versions:
```

```
// Description:
```

//

```
// Dependencies:
```

//

```
// Revision:
```

```
// Revision 0.01 - File Created
```

// Additional Comments:

//

////////////////////////////////////

```

module ALUMux(

    input [31:0] eqb,    // Input B data from the ALU

    input [31:0] eimm32, // Immediate value from the pipeline

    input ealuimm,      // Mux control signal

    output reg [31:0] b // Output data selected by the Mux

);

always @(*) begin

    case(ealuimm)

        1'b0: // Select eqb as the output

            begin

                b <= eqb; // Select eqb when ealuimm is 0.

            end

        1'b1: // Select eimm32 as the output

            begin

                b <= eimm32; // Select eimm32 when ealuimm is 1.

            end

    endcase

end

endmodule

`timescale 1ns / 1ps

```

//

// Company:

// Engineer:

//

// Create Date: 04/07/2024 10:08:06 PM

// Design Name:

// Module Name: EXEMempipeline_dp

// Project Name:

// Target Devices:

// Tool Versions:

// Description:

//

// Dependencies:

//

// Revision:

// Revision 0.01 - File Created

// Additional Comments:

//

//

module EXEMEMpipeline(

input ewreg, // Control signal for writing to the register file

```

input em2reg,      // Control signal for writing to the register file (Memory stage)
input ewmem,      // Control signal for writing to memory
input [4:0] edestReg, // Destination register address
input [31:0] r,    // Result from the ALU
input [31:0] eqb,  // Value from source register B
input clk,        // Clock signal

output reg mwreg,  // Output for write enable signal
output reg mm2reg, // Output for write enable signal (M2 stage)
output reg mwmem,  // Output for memory write enable signal
output reg [4:0] mdestReg, // Output for destination register address
output reg [31:0] mr, // Output for result from the ALU
output reg [31:0] mqb // Output for value from source register B
);

```

```

always @ (posedge clk)

```

```

begin

```

```

    mwreg = ewreg;      // Update write enable signal for register file writing.

```

```

    mm2reg = em2reg;    // Update write enable signal for register file writing in M2
stage.

```

```

    mwmem = ewmem;      // Update memory write enable signal.

```

```

    mdestReg = edestReg; // Update destination register address.

```

```

    mr = r;             // Update result from the ALU.

```

```
    mqb = eqb;          // Update value from source register B.  
end
```

```
endmodule
```

```
`timescale 1ns / 1ps
```

```
////////////////////////////////////////////////////////////////
```

```
// Company:
```

```
// Engineer:
```

```
//
```

```
// Create Date: 04/07/2024 10:09:58 PM
```

```
// Design Name:
```

```
// Module Name: MEM_DataMemory_dp
```

```
// Project Name:
```

```
// Target Devices:
```

```
// Tool Versions:
```

```
// Description:
```

```
//
```

```
// Dependencies:
```

```
//
```

```
// Revision:
```

```
// Revision 0.01 - File Created
```

```
// Additional Comments:
```

```
//
```

```
////////////////////////////////////////////////////////////////
```

```
module DataMemory(
```

```
    input [31:0] mr,    // Memory read address
```

```
    input [31:0] mqb,   // Data to be written to memory
```

```
    input mwmem,        // Memory write control signal
```

```
    input clk,          // Clock signal
```

```
    output reg [31:0] mdo // Data read from memory
```

```
);
```

```
// Define a data memory array with 64 words
```

```
reg [31:0] dataMemory [0:63];
```

```
// Initialize data memory with some values (words 0-9)
```

```
initial begin
```

```
    dataMemory[0] = 32'hA00000AA;
```

```
    dataMemory[1] = 32'h10000011;
```

```
    dataMemory[2] = 32'h20000022;
```

```
    dataMemory[3] = 32'h30000033;
```

```
    dataMemory[4] = 32'h40000044;
```

```
    dataMemory[5] = 32'h50000055;
```

```

dataMemory[6] = 32'h60000066;
dataMemory[7] = 32'h70000077;
dataMemory[8] = 32'h80000088;
dataMemory[9] = 32'h90000099;
end

always @(*) begin
    // Set mdo to the value at the memory read address (bits 7:2 of mr)
    mdo = dataMemory[mr[7:2]]; // Read data from memory at the specified address.
end

always @(negedge clk) begin
    //If mwmem is 1, write the value in mqb to the memory at the read address
    if (mwmem == 1) begin
        dataMemory[mr[7:2]] <= mqb; // Write data to memory at the specified address.
    end
end

endmodule

`timescale 1ns / 1ps

////////////////////////////////////

// Company:

```



```
// Engineer:
//
// Create Date: 04/07/2024 10:09:58 PM
// Design Name:
// Module Name: MEM_DataMemory_dp
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
////////////////////////////////////////////////////////////////
```

```
module DataMemory(
    input [31:0] mr,    // Memory read address
    input [31:0] mqb,   // Data to be written to memory
    input mwmem,        // Memory write control signal
```

```

input clk,          // Clock signal

output reg [31:0] mdo // Data read from memory

);

// Define a data memory array with 64 words
reg [31:0] dataMemory [0:63];

// Initialize data memory with some values (words 0-9)
initial begin
    dataMemory[0] = 32'hA00000AA;
    dataMemory[1] = 32'h10000011;
    dataMemory[2] = 32'h20000022;
    dataMemory[3] = 32'h30000033;
    dataMemory[4] = 32'h40000044;
    dataMemory[5] = 32'h50000055;
    dataMemory[6] = 32'h60000066;
    dataMemory[7] = 32'h70000077;
    dataMemory[8] = 32'h80000088;
    dataMemory[9] = 32'h90000099;
end

always @(*) begin
    // Set mdo to the value at the memory read address (bits 7:2 of mr)

```

```

        mdo = dataMemory[mr[7:2]]; // Read data from memory at the specified address.
    end

    always @(negedge clk) begin
        //If mwmem is 1, write the value in mqb to the memory at the read address
        if (mwmem == 1) begin
            dataMemory[mr[7:2]] <= mqb; // Write data to memory at the specified address.
        end
    end

end

endmodule

```

Testbench:

```

module TestBench;

    reg clk;

    wire [31:0] pc;
    wire [31:0] dinstOut;
    wire ewreg;
    wire em2reg;
    wire ewmem;
    wire [3:0] ealuc;

```

```
wire ealuimm;  
  
wire [4:0] edestReg;  
  
wire [31:0] eqa;  
  
wire [31:0] eqb;  
  
wire [31:0] eimm32;
```

```
wire mwreg;  
  
wire mm2reg;  
  
wire mwmem;  
  
wire [4:0] mdestReg;  
  
wire [31:0] mr;  
  
wire [31:0] mqb;
```

```
wire wwreg;  
  
wire wm2reg;  
  
wire [4:0] wdestReg;  
  
wire [31:0] wr;  
  
wire [31:0] wdo;
```

```
initial begin  
  
    clk <= 1'b0;
```

end

Datapath datapath(

.clk(clk),

.pc(pc),

.dinstOut(dinstOut),

.ewreg(ewreg),

.em2reg(em2reg),

.ewmem(ewmem),

.ealuc(ealuc),

.ealuimm(ealuimm),

.edestReg(edestReg),

.eqa(eqa),

.eqb(eqb),

.eimm32(eimm32),

.mwreg(mwreg),

.mm2reg(mm2reg),

.mwmem(mwmem),

.mdestReg(mdestReg),

.mr(mr),

.mqb(mqb),

.wwreg(wwreg),

.wm2reg(wm2reg),

```
.wdestReg(wdestReg),  
.wr(wr),  
.wdo(wdo)  
);
```

```
always begin  
    #10;  
    clk = ~clk;  
end
```

```
endmodule
```