


Lab 1

CMPEN 331


Sethu Senthil

1/11/2024


Waveform:

 


Schematic:

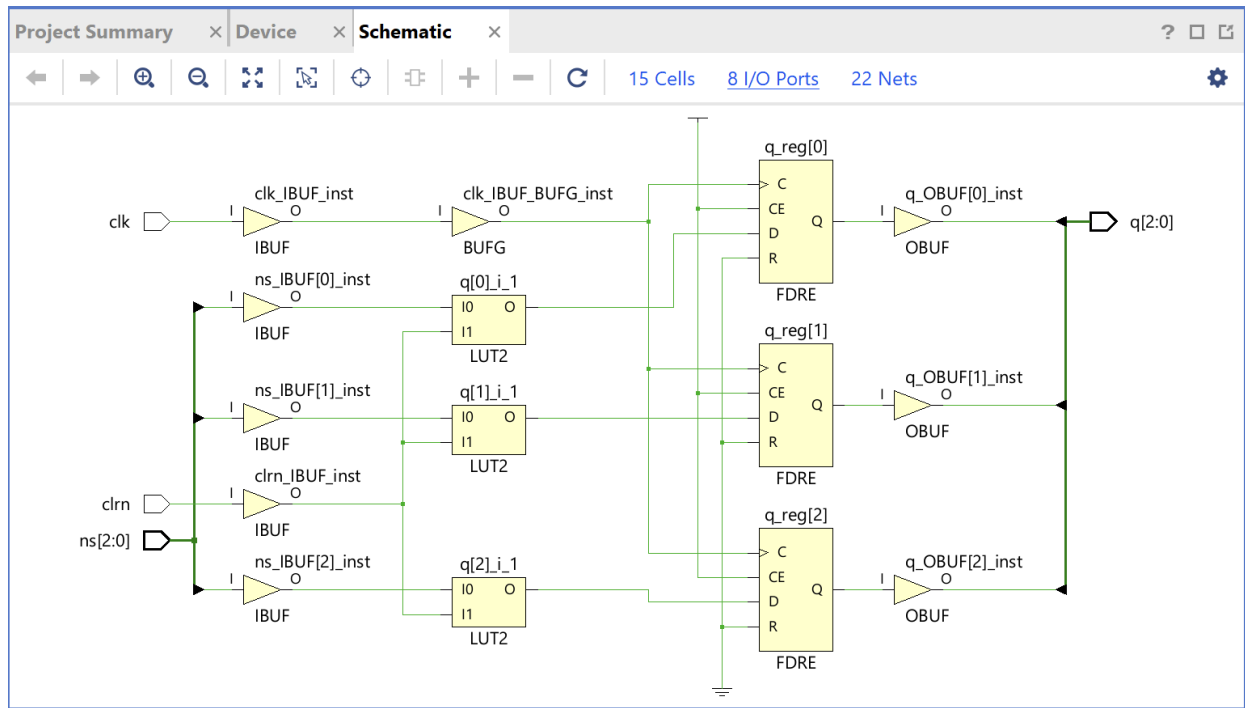

IO Planning:

 

Floor Planning:

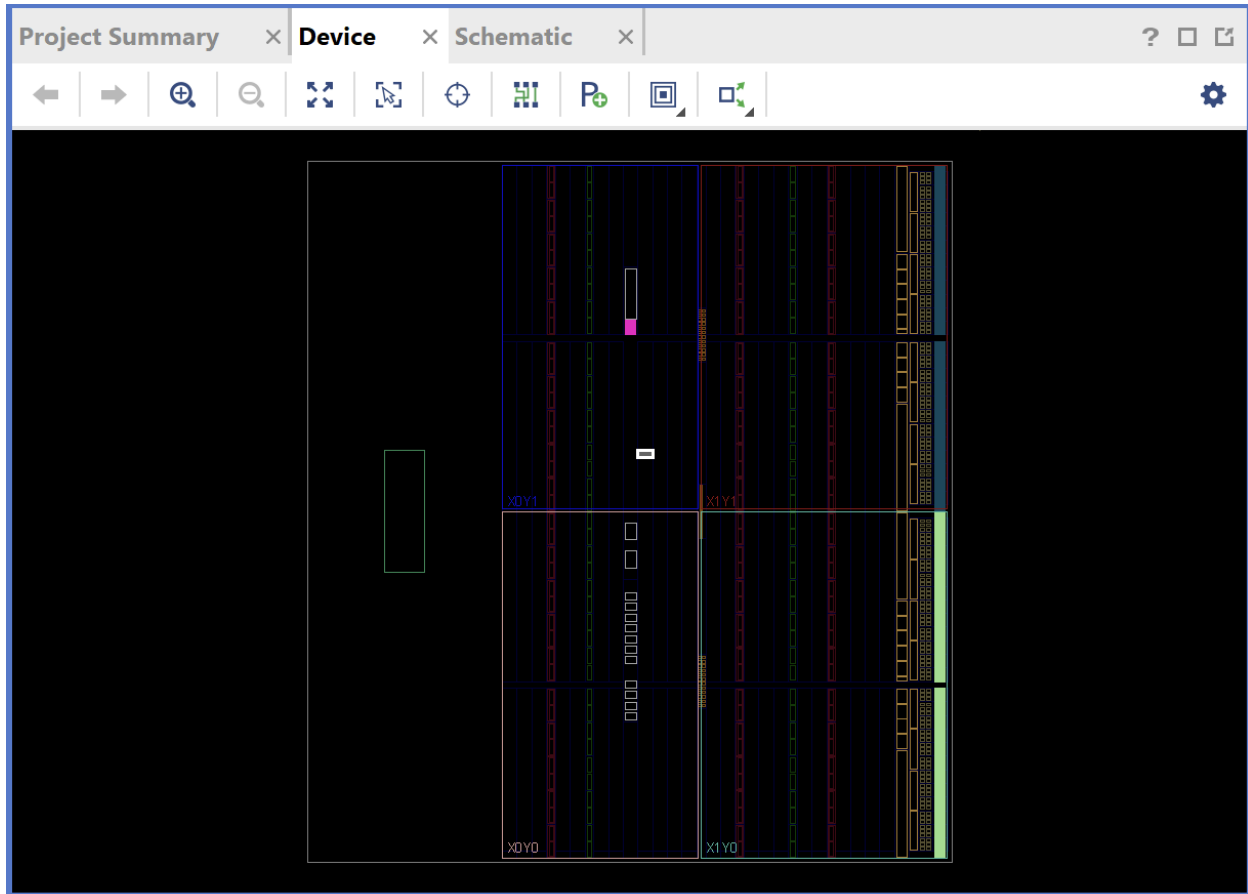

Code:

Module:

```
`timescale 1ns / 1ps
```

```
////////////////////////////////////////////////////////////////
```

```
// Company:
```

```
// Engineer:
```

```
//
```

```
// Create Date: 05/18/2020 12:08:45 PM
```

```
// Design Name:
```

```
// Module(s) Name: dff3 and counter
```

```
// Project Name: 7 segment display
```

```
// Target Devices:
```

```
// Tool Versions:
```

```
// Description:
```

```
//
```

```
// Dependencies:
```

```
//
```

```

// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
/////////////////////////////////////////////////////////////////

// Module    : D flip-flop
// Description : At the positive edge of the clock, set the current state based on the clear
// Input(s)   : 3-bit Next State, Clear and Clock
// Output(s)  : 3-bit Current State
module dff3(input [2:0] ns, input clrn, input clk, output reg [2:0] q);
    always @(posedge clk)
        begin
            if (clrn == 1) begin
                q <= ns;
            end
            else begin
                q <= 3'b000;
            end
        end
    end
endmodule

// Module    : Up/Down Counter
// Description : Combinational circuit that generates the next state and LED control signals
// based on input u
// Input(s)   : 3-bit Current State, 1-bit u
// Output(s)  : 3-bit Next State, 7 1-bit segments of the LED
module counter(input [2:0] q, input u, output reg [2:0] ns,
    output reg a, output reg b, output reg c, output reg d, output reg e, output reg f, output reg g
);
    always @(*)
        begin
            if (u == 1) begin
                if (q == 3'b101) begin
                    ns <= 3'b000;
                end
                else begin
                    ns <= q + 1;
                end
            end
            else begin
                if (q == 3'b000) begin
                    ns <= 3'b101;
                end
            end
        end
    end
endmodule

```

```

        else begin
            ns <= q - 1;
        end
    end
case(q)
    3'b000: begin
        g=1'b1; f=1'b0; e=1'b0; d=1'b0; c=1'b0; b=1'b0; a=1'b0;
    end
    3'b001: begin
        g=1'b1; f=1'b1; e=1'b1; d=1'b1; c=1'b0; b=1'b0; a=1'b1;
    end
    3'b010: begin
        g=1'b0; f=1'b1; e=1'b0; d=1'b0; c=1'b1 ;b=1'b0; a=1'b0;
    end
    3'b011: begin
        g=1'b0; f=1'b1; e=1'b1; d=1'b0; c=1'b0; b=1'b0; a=1'b0;
    end
    3'b100: begin
        g=1'b0; f=1'b0; e=1'b1; d=1'b1; c=1'b0; b=1'b0; a=1'b1;
    end
    3'b101: begin
        g=1'b0; f=1'b0; e=1'b1; d=1'b0; c=1'b0; b=1'b1; a=1'b0;
    end
endcase
end
endmodule

```

Testbench:

```
`timescale 1ns / 1ps
```

```
////////////////////////////////////////////////////////////////
```

```
// Company:
```

```
// Engineer:
```

```
//
```

```
// Create Date: 05/18/2020 12:08:45 PM
```

```
// Design Name:
```

```
// Module(s) Name: dff3 and counter
```

```
// Project Name: 7 segment display
```

```
// Target Devices:
```

```
// Tool Versions:
```

```
// Description:
```

```
//
```

```
// Dependencies:
```

```

//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
////////////////////////////////////

// Module    : D flip-flop
// Description : At the positive edge of the clock, set the current state based on the clear
// Input(s)   : 3-bit Next State, Clear and Clock
// Output(s)  : 3-bit Current State
module dff3(input [2:0] ns, input clrn, input clk, output reg [2:0] q);
    always @ (posedge clk)
        begin
            if (clrn == 1) begin
                q <= ns;
            end
            else begin
                q <= 3'b000;
            end
        end
    end
endmodule

// Module    : Up/Down Counter
// Description : Combinational circuit that generates the next state and LED control signals
// based on input u
// Input(s)   : 3-bit Current State, 1-bit u
// Output(s)  : 3-bit Next State, 7 1-bit segments of the LED
module counter(input [2:0] q, input u, output reg [2:0] ns,
    output reg a, output reg b, output reg c, output reg d, output reg e, output reg f, output reg g
);
    always @(*)
        begin
            if (u == 1) begin
                if (q == 3'b101) begin
                    ns <= 3'b000;
                end
                else begin
                    ns <= q + 1;
                end
            end
            else begin
                if (q == 3'b000) begin
                    ns <= 3'b101;
                end
            end
        end
    end
endmodule

```

```

        end
    else begin
        ns <= q - 1;
    end
end
case(q)
    3'b000: begin
        g=1'b1; f=1'b0; e=1'b0; d=1'b0; c=1'b0; b=1'b0; a=1'b0;
    end
    3'b001: begin
        g=1'b1; f=1'b1; e=1'b1; d=1'b1; c=1'b0; b=1'b0; a=1'b1;
    end
    3'b010: begin
        g=1'b0; f=1'b1; e=1'b0; d=1'b0; c=1'b1 ;b=1'b0; a=1'b0;
    end
    3'b011: begin
        g=1'b0; f=1'b1; e=1'b1; d=1'b0; c=1'b0; b=1'b0; a=1'b0;
    end
    3'b100: begin
        g=1'b0; f=1'b0; e=1'b1; d=1'b1; c=1'b0; b=1'b0; a=1'b1;
    end
    3'b101: begin
        g=1'b0; f=1'b0; e=1'b1; d=1'b0; c=1'b0; b=1'b1; a=1'b0;
    end
endcase
end
endmodule

```